

ECE 551

Digital Design And Synthesis

Fall '16

Simulator Mechanics

Testbench Basics (stimulus generation)

Dataflow Verilog

Administrative Matters



- HW2 will be posted soon. HW1 due on Wednesday 9/21
- Purchase of DEo Nano boards (1 per every 2 people)
 - New/used ones available from Steve Manthey (copy center, EH2415, across from ECE department office)
 - Look for an email and moodle post with details
- Watch Videos on rest of Lecture03 materials

Analog Simulation (Spice Engine)



- Divide “time” into slices
- Update information in whole circuit at each slice
- Used by SPICE
- Allows detailed modeling of current and voltage
- Computationally intensive and slow
- Don't need this level of detail for most digital logic simulation

Digital Simulation

  - Could update every signal on an input change




  - Could update just the full path on input change





- Don't even need to do that much work!

Event-Driven Simulation

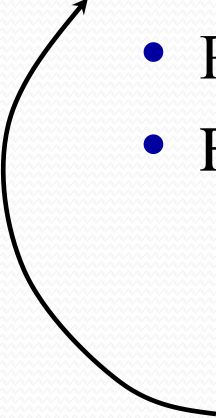- When an input to the simulating circuit changes, put it on a “changed” list
 - Loop while the “changed” list isn’t empty:
 - Remove a signal from the “changed” list
 - For each sink of the signal
 - ✓ Recompute its new output(s)
 - ✓ For any output(s) that have changed value, add that signal to the “changed” list
 - When the “changed” list is empty:
 - Keep simulation results
 - Advance simulation time to next stimulus (input) event
- 

Simulation


- Update only if changed

  


- Some circuits are very large
 - Updating every signal => very slow simulation
 - Event-driven simulation is much faster!

Testbench Basics (stimulus generation)

 
- Need to verify your design
 - “Design Under Test” (DUT)
- Use a “testbench”
 - Verilog module with no ports
 - Generates or routes inputs to the DUT
 - For now we will monitor outputs via human interface



OR

 


Simulation Example

 

Our DUT is a simple 4-bit adder, with carry in and carry out

Use a consistent naming convention for your test benches:

 I usually add `_tb` to the end of the unit name



adder4bit_tb

Testbench Requirements

- Instantiate the unit being tested (DUT)
- Provide input to that unit
 - Usually a number of different input combinations!
- Watch the “results” (outputs of DUT)
 - Can watch ModelSim Wave window...
 - Can print out information to the screen or to a file
- This way of monitoring outputs (human interface) is dangerous & incomplete.
 - Subject to human error
 - Cannot be automated into batch jobs (regression suite)
 - Self checking testbenches will be covered later

Output Test Info

- Several different system calls to output info
 - `$monitor`
 - Output the given values whenever one changes
 - Can use when simulating Structural, RTL, and/or Behavioral
 - `$display`, `$strobe`
 - Output specific information like a `printf` in a C program
 - Used in Behavioral Verilog
- Can use formatting strings with these commands
- Only means anything in simulation
- Ignored by synthesizer

Output Format Strings

- Formatting string
 - %h, %H hex
 - %d, %D decimal
 - %o, %O octal
 - %b, %B binary
 - %t time
- \$monitor(“%t: %b %h %h %h %b\n”,
 \$time, c_out, sum, a, b, c_in);
- Can get more details from Verilog standard

Output Example

```
module adder4bit_tb;
  reg[8:0] stim;
  wire[3:0] S;
  wire C4;

  // inputs to DUT are regs
  // outputs of DUT are wires

  // instantiate DUT
  adder4bit(.sum(S), .c_out(C4), .a(stim[8:5]), .b(stim[4:1]), .c(stim[0]));

  initial $monitor("%t A:%h B:%h ci:%b Sum:%h co:%b\n", $time,
    stim[8:5], stim[4:1], stim[0], C4, S);

  // stimulus generation
  initial begin
    stim = 9'b0000_0000_0; // at 0 ns
    #10 stim = 9'b1111_0000_1; // at 10 ns
    #10 stim = 9'b0000_1111_1; // at 20 ns
    #10 stim = 9'b1111_0001_0; // at 30 ns
    #10 stim = 9'b0001_1111_0; // at 40 ns
    #10 $stop; // at 50 ns – stops simulation

  end
endmodule
```

Generating Clocks

- Wrong way:

```
initial begin
```

```
    #5 clk = 0;
```

```
    #5 clk = 1;
```

```
    #5 clk = 0;
```

```
    ... (repeat hundreds of times)
```

```
end
```

- Right way:

```
initial clk = 0;
```

```
always
```

```
    #5 clk = ~clk;
```

```
initial begin
```

```
    clk = 0;
```

```
    forever #5 clk = ~clk;
```

```
end
```

LESS TYPING

- Easier to read, harder to make mistake

Exhaustive Testing

- For combinational designs w/ up to 8 or 9 inputs
 - Test ALL combinations of inputs to verify output
 - Could enumerate all test vectors, but don't...
 - Generate them using a “for” loop!

```
reg [4:0] x;  
initial begin  
    for (x = 0; x < 16; x = x + 1)  
        #5;    // need a delay here!  
end
```

- Need to use “reg” type for loop variable? Why?

Why Loop Vector Has Extra Bit

- Want to test all vectors 0000 to 1111
 reg [3:0] x;
 initial begin
 for (x = 0; x < 16; x = x + 1)
 #5; // need a delay here!
 end
- If x is 4 bits, it only gets up to 1111 => 15
 - 1100 => 1101 => 1110 => 1111 => 0000 => 0001
- x is never >= 16... so loop goes forever

Example: DUT

```
module Comp_4 (A_gt_B, A_lt_B, A_eq_B, A, B);  
output A_gt_B, A_lt_B, A_eq_B;  
input   [3:0] A, B;  
    // Code to compare A to B  
    // and set A_gt_B, A_lt_B, A_eq_B accordingly  
endmodule
```

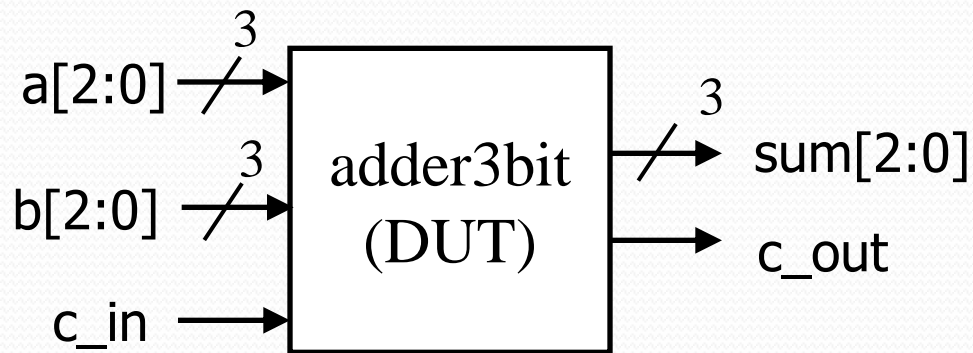

Example: Testbench

```
module Comp_4_tb();  
wire    A_gt_B, A_lt_B, A_eq_B;  
reg     [4:0] A, B;                                // sized to prevent loop wrap around  
  
Comp_4 M1 (A_gt_B, A_lt_B, A_eq_B, A[3:0], B[3:0]);    // DUT  
  
initial $monitor("%t A: %h B: %h AgtB: %b AltB: %b AeqB: %b",  
    $time, A[3:0], B[3:0], A_gt_B, A_lt_B, A_eq_B);  
  
initial #2000 $finish;                                // end simulation, quit program  
  
initial begin  
#5 for (A = 0; A < 16; A = A + 1) begin                // exhaustive test of inputs  
    for (B = 0; B < 16; B = B + 1) begin #5; // may want to test x's and z's  
    end // first for  
    end // second for  
end // initial  
endmodule
```


*note multiple
initial blocks*

Do ModelSim Example Here

- ModelSim Example of 3-bit wide adder block



Stimulus for Sequential Circuits

 

- Imagine an 8-bit counter with an active low reset signal.
- When `en=0` the count is frozen
- The counter counts up if `up_dwn_n=1` or down if `up_dwn_n=0`

- What should the testbench look like?
- How should the stimulus be generated?

Stimulus for Sequential Circuits

```
module up_dwn_tb();

logic clk, rst_n;
logic en, up_dwn_n;

// Instantiate DUT //
up_dwn iDUT(.clk(clk), .rst_n(rst_n), .en(en), .up_dwn(up_dwn_n));

initial begin
    clk = 0;
    rst_n = 0;           // assert reset
    en = 0;              // start with it disabled
    up_dwn_n = 1;        // count up at first
    #16 rst_n = 1;       // deassert clock
    #5 en = 1;           // start counting
    #50 en = 0;          // stop after 5 clocks
    #10 en = 1;          // start after 1 clock freeze
    #20 up_dwn_n = 0;    // start counting down
end

always
    #5 clk = ~clk;

endmodule
```

- Can do it using delays as shown here.
- Signal timings are calculated based on your clock period
- Figuring it out is a pain
- What if you want to change the clock period?
- There is a better way

Stimulus for Sequential Circuits

```
module up_dwn_tb();

logic clk, rst_n;
logic en, up_dwn_n;

// Instantiate DUT //
up_dwn iDUT(.clk(clk), .rst_n(rst_n), .en(en), .up_dwn_n

initial begin
    clk = 0;
    rst_n = 0; // assert reset
    en = 0; // start with it disabled
    up_dwn_n = 1; // count up at first
    @(posedge clk); // wait one clock cycle
    @(negedge clk) rst_n = 1; // deassert reset on negative
    @(posedge clk) en = 1; // start counting
    repeat (5) @(posedge clk); // wait 5 clock cycles
    en = 0; // stop counting
    @(posedge clk) en = 1; // for 1 clock cycle
    repeat (2) @(posedge clk); // wait 2 clock cycles
    up_dwn_n = 0; // start counting backwards
end

always
    #5 clk = ~clk;
```

- Can use clock edges as trigger for stimulus events
- Easier to think about, no arithmetic with clock period
- Code is independent of clock period
- Can use repeat() loop to wait a given number of clocks


FSM Testing

- Response to input vector depends on state
- For each state:
 - Check all transitions
 - Check output for each transition
 - This includes any transitions back to same state!
- Can be time consuming to traverse FSM repeatedly...

 Example : Gray Code Counter – Test1 *(the instructor is a chicken)*

- Write a testbench to test a gray code counter
module gray_counter(out, clk, rst);
- Rst in this case is a synchronounous reset
 - It does not directly asynchronously reset the flops
 - It is an input to the combinational logic that sets the next state to all o's.
- Initially reset the counter and then test all states, but do not test reset in each state.

Bubble Diagram of 3-bit Gray Code “State Machine”



Solution : Gray Code Counter – Test1

```
module t1_gray_counter();  
  wire [2:0] out;  
  reg   clk, rst;  
  gray_counter GC(out, clk, rst); // DUT  
  
  initial $monitor("%t out: %b rst: %b ", $time, out, rst); // no clock  
  initial #100 $finish;           // end simulation, quit program  
  
  initial begin  
    clk = 0;  
    rst = 1;  
    #10 rst = 0;           // release reset after first clock rise and let run  
  end  
  
  always  
    #5 clk = ~clk;        // clock rising edges at 5,15,25,...  
  
endmodule
```

Simulation: Gray Code Counter – Test1

#	0	out: xxx	rst: 1	// reset system
#	5	out: 000	rst: 1	// first positive edge
#	10	out: 000	rst: 0	// release reset
#	15	out: 001	rst: 0	// traverse states
#	25	out: 011	rst: 0	
#	35	out: 010	rst: 0	
#	45	out: 110	rst: 0	
#	55	out: 111	rst: 0	
#	65	out: 101	rst: 0	
#	75	out: 100	rst: 0	
#	85	out: 000	rst: 0	
#	95	out: 001	rst: 0	

Force/Release In Testbenches

- Allows you to “override” value FOR SIMULATION
- Doesn’t do anything in “real life”
- How does this help testing?
 - Can help to pinpoint bug
 - Can use with FSMs to override state
 - Force to a state
 - Test all transitions/outputs for that state
 - Force the next state to be tested, and repeat
- Can help achieve code coverage (*more on that later*)

Force/Release Example


```
assign y = a & b;  
assign z = y | c;  
initial begin  
    a = 0; b = 0; c = 0;  
    #5 a = 0; b = 1; c = 0;  
    #5 force y = 1;  
    #5 b = 0;  
    #5 release y;  
    #5 $stop;  
end
```

T	a	b	c	y	z
0	0	0	0	0	0
5	0	1	0	0	0
10	0	1	0	1	1
15	0	0	0	1	1
20	0	0	0	0	0

 Example : Gray Code Counter – Test2

- Write a testbench to exhaustively test the gray code counter example above
module gray_counter(out, clk, rst);
- Initially reset the counter and then test all states, then test reset in each state.
- Remember that in this example, rst is treated as an input to the combinational logic.
- Thoroughly

Bubble Diagram of 3-bit Gray Code “State Machine”



Example : Gray Code Counter – Test2

```
module t2_gray_counter();  
  wire [2:0] out;  
  reg   clk, rst;  
  gray_counter GC(out, clk, rst); // DUT
```

```
  initial $monitor("%t out: %b rst: %b ", $time, out, rst); // no clock  
  initial #300 $finish; // end simulation, quit program
```

```
  initial begin
```

```
    clk = 0; forever #5 clk = ~clk; // What is the clock period?
```

```
  end
```

```
  initial begin
```

```
    rst = 1; #10 rst = 0;
```

```
    #90 rst = 1; force GC.ns = 3'b001; #10 release GC.ns;
```

```
    #10 force GC.ns = 3'b001; #10 release GC.ns;
```


```
    #10 force GC.ns = 3'b010; #10 release GC.ns;
```

```
    ...
```

```
  end // initial
```

```
endmodule
```

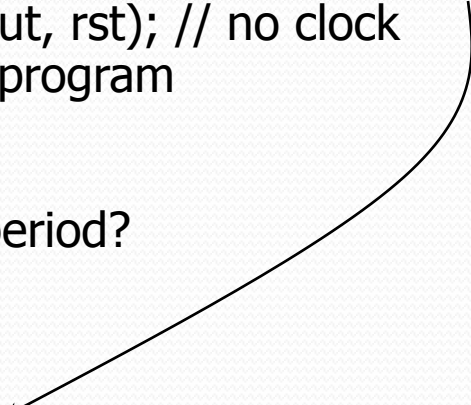Note the Use of hierarchical Naming to get at the internal Signals. This is a very handy thing in testbenches.



Simulation: Gray Code Counter – Test2

# 0 out: xxx rst: 1	# 100 out: 001 rst: 1	# 215 out: 000 rst: 1
# 5 out: 000 rst: 1	# 105 out: 000 rst: 1	# 225 out: 101 rst: 1
# 10 out: 000 rst: 0	// at #115 out = 000	# 235 out: 000 rst: 1
# 15 out: 001 rst: 0	# 125 out: 001 rst: 1	# 245 out: 100 rst: 1
# 25 out: 011 rst: 0	# 135 out: 000 rst: 1	# 255 out: 000 rst: 1
# 35 out: 010 rst: 0	# 145 out: 011 rst: 1	
# 45 out: 110 rst: 0	# 155 out: 000 rst: 1	
# 55 out: 111 rst: 0	# 165 out: 010 rst: 1	
# 65 out: 101 rst: 0	# 175 out: 000 rst: 1	
# 75 out: 100 rst: 0	# 185 out: 110 rst: 1	
# 85 out: 000 rst: 0	# 195 out: 000 rst: 1	
# 95 out: 001 rst: 0	# 205 out: 111 rst: 1	

Dataflow Verilog

- The continuous **assign** statement
 - It is the main construct of Dataflow Verilog
 - It is deceptively powerful & useful
- Generic form:

```
assign [drive_strength] [delay] list_of_net_assignments;
```

Where:

`list_of_net_assignment ::= net_assignment [{,net_assignment}]`

& Where:

`Net_assignment ::= net_lvalue = expression`

OK...that means just about nothing to me...how about some examples?

Continuous Assign Examples

- Simplest form:

```
// out is a net, a & b are also nets  
assign out = a & b; // and gate functionality
```

- Using vectors

```
wire [15:0] result, src1, src2; // 3 16-bit wide vectors  
assign result = src1 ^ src2; // 16-bit wide XOR
```

- Can you implement a 32-bit adder in a single line?

```
wire [31:0] sum, src1, src2; // 3 32-bit wide vectors  
assign {c_out,sum} = src1 + src2 + c_in; // wow!
```

What is this?

Vector concatenation

- Can “build” vectors using smaller vectors and/or scalar values
- Use the {} operator
- Example 1

```
module concatenate(out, a, b, c, d);  
  input [2:0] a;  
  input [1:0] b, c;  
  input d;  
  output [9:0] out;  
  
  assign out = {a[1:0],b,c,d,a[2]};  
  
endmodule
```

*becomes
8-bit vector:*


$a_1a_0b_1b_0c_1c_0da_2$



Vector concatenation

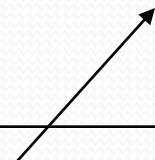- Example 2

```
module add_concatenate(out, a, b, c, d);  
  input [7:0] a;  
  input [4:0] b;  
  input [1:0] c;  
  input d;  
  output [7:0] out;  
  
  add8bit(.sum(out), .cout(), .a(a), .b({b,c,d}), .cin());  
  
endmodule
```



- Vector concatenation is not limited to assign statements. In this example it is done in a port connection of a module instantiation.

Replication within Concatenation

- Sometimes it is useful to replicate a bit (or vector) within the concatenation of another vector.
 - This is done with a replication constant (number) in front of the {}
 - Example: (sign extend an 8-bit value to a 16bit bus)

```
input [7:0] offset; // 8-bit offset term from EEPROM
```


```
wire [15:0] src1; // 16-bit source busses to ALU
```

```
assign src1 = {{8{offset[7]}},offset}; // sign extend offset term
```

- Recall, to sign extend a 2's complement number you just replicate the MSB.
 - In this example the MSB of the 8-bit offset term has to be replicated 8 times to flush out to a full 16-bit value

Back to the Continuous Assign

- More basic generic form:
 `assign <LHS> = <RHS expression>;`
- If RHS result changes, LHS is updated with new value
 - Constantly operating (“continuous”)
 - It's **hardware!**
- RHS can use operators (i.e. +, -, &, |, ^, ~, >>, ...)

 

```
assign {c_out,sum} = src1 + src2 + c_in;
```

Operators: Arithmetic

- Much easier than structural!

*	multiply	**	exponent
/	divide	%	modulus
+	add	-	subtract

- Some of these don't synthesize
- Also have unary operators +/- (pos/neg)
- Understand bitsize!
 - Can affect sign of result
 - Is affected by bitwidth of BOTH sides
 $\text{Prod}[7:0] = a[3:0] * b[3:0]$

Operators

- Shift (<<, >>, <<<, >>>)
- Relational (<, >, <=, >=)
- Equality (==, !=, ===, !==)
 - ===, !== test x's, z's! ONLY USE FOR testbenches
- Logical Operators (&&, ||, !)
 - Build clause for if statement or conditional expression
 - Returns single bit values
- Bitwise Operators (&, |, ^, ~)
 - Applies bit-by-bit!
- Watch ~ vs !, | vs. ||, and & vs. &&

Reduction Operators

- Reduction operators reduce all the bits of a vector to a single bit by performing an operation across all bits.
 - Reduction AND
 - ✓ `assign all_ones = &accumulator; // are all bits set?`
 - Reduction OR
 - ✓ `assign not_zero = |accumulator; // are any bits set?`
 - Reduction XOR
 - ✓ `assign parity = ^data_out; // even parity bit`

Lets Kick up the Horse Power

- You thought a 32-bit adder in one line was powerful. Lets try a 32-bit MAC...

Design a multiply-accumulate (MAC) unit that computes

$$Z[31:0] = A[15:0] * B[15:0] + C[31:0]$$

It sets overflow to one, if the result cannot be represented using 32 bits.

```
module mac(output Z [31:0], output overflow,  
           input [15:0] A, B, input [31:0] C);
```

Lets Kick up the Horse Power

```
module mac(output Z [31:0], output overflow,  
           input [15:0] A, B, input [31:0] C);  
    assign {overflow, Z} = A*B + C;  
endmodule
```

I am a brilliant genius. I am a HDL coder extraordinaire. I created a 32-bit MAC, and I did it in a single line.

assign {overflow, Z} = A*B + C;

Oh my god,
I've created a
monster

Synopsys



Conditional Operator

- This is a favorite!
 - The functionality of a 2:1 Mux
 - `assign out = conditional_expr ? true_expr : false_expr;`

Examples:

```
// a 2:1 mux
```

```
assign out = select ? in1 : in0;
```


```
// tri-state bus
```

```
assign src1 = rf2src1 ? Mem[addr1] : 16'hzzzz;
```

```
// Either true_expr or false_expr can also be a conditional operator
```

```
// lets use this to build a 4:1 mux
```
 
```
assign out = sel[1] ? (sel[0] ? in3 : in2) : (sel[0] ? in1 : in0);
```



Conditional assign (continued)

Examples: (nesting of conditionals)

```
localparam add    = 3'b000
localparam and    = 3'b001
localparam xor     = 3'b010
localparam shift_l = 3'b011
localparam shift_r = 3'b100
```

// an ALU capable of arithmetic, logical, shift, and zero

```
assign {cout,dst} = (op==add)    ?    src1+src2+cin :
                    (op==and)    ?    {1'b0,src1 & src2} :
                    (op==xor)    ?    {1'b0,src1 ^ src2} :
                    (op==shift_l) ?    {src1,cin} :
                    (op==shift_r) ?    {src1[0],src1[15],src1[15:1]} :
                                   17'h00000;
```

This can be very confusing to read if
not coded with proper formatting

System Verilog for ALU

```
module simp_alu(src1,src2,cin,op,dst,cout);

typedef enum logic [2:0] {ADD, AND, XOR, SHFT_L, SHFT_R} op_t;

input [15:0] src1,src2;    // input busses
input cin;                // carry in
input [2:0] op;           // operation select

output [15:0] dst;        // result of ALU
output cout;             // carry output

op_t op_i;

assign op_i = op_t'(op);

// an ALU capable of arithmetic, logical, shift, and zero
assign {cout,dst} = (op_i==ADD)    ?  src1+src2+cin :
                  (op_i==AND)    ?  {1'b0,src1 & src2} :
                  (op_i==XOR)    ?  {1'b0,src1 ^ src2} :
                  (op_i==SHFT_L) ?  {src1[15:1],src1[0]} :
                  (op_i==SHFT_R) ?  {src1[15],src1[14:0]} :
                  0;

endmodule
```

Again, system verilog allows for the use of enumerated types.

Does not make the code more readable, but does enhance debug because of waveform view.

/dst	16'hffff	16'hffff	16'h0000	16'hffff
/op	XOR	ADD	AND	XOR
/src1	16'h5555	16'h5555		
/src2	16'haaaa	16'haaaa		

A Few Other Possibilities

- The implicit assign
 - Goes in the wire declaration
wire [3:0] sum = a + b;
 - Can be a useful shortcut to make code succinct, but doesn't allow fancy LHS combos
assign {cout, sum} = a + b + cin;
- Personal choice
 - ✓ You are welcome to use it when appropriate (I never do)

Implicit Net Declarations

- When wire is used but not declared, it is *implied*

```
module majority(output out, input a, b, c);  
    assign part1 = a & b;  
    assign part2 = a & c;  
    assign part3 = b & c;  
    assign out = part1 | part2 | part3;  
endmodule
```

- Defaults to single bit wire
- Breaks compatibility with some tools
- Disable by using ``default_nettype none` directive
 - ✓ Helps to avoid wasting time on typos

Latches with Continuous Assign

- What does the following statement imply/do?


assign q_out = enable ? data_in : q_out;

- It acts as a latch. If enable is high new data goes to q_out. Otherwise q_out maintains its previous value.
- Ask yourself...Is that what I meant when I coded this?
- It simulates fine...just like a latch


Latches with Continuous Assign

```
assign q_out = enable ? data_in : q_out;
```

- How does it synthesize??

 

 Is the synthesizer smart enough to see this as a latch and pick a latch element from the standard cell library?



Or is it what you code is what you get? A combinational feedback loop. Still acts like a latch. Do you feel comfortable with this?